

Q. Simplify $Y = \overline{AB + \bar{A} + AB}$

Ans $Y = (\overline{AB}) \cdot (\bar{\bar{A}}) \cdot (\overline{AB})$

$$Y = AB \cdot A \cdot (\bar{A} + \bar{B})$$

$$Y = ABA \cdot (\bar{A} + \bar{B})$$

$$[\because AA = A]$$

$$Y = AAB \cdot (\bar{A} + \bar{B})$$

$$Y = (AB)(\bar{A} + \bar{B}) \Rightarrow AB\bar{A} + AB\bar{B}$$

$$Y = A\bar{A}B + AB\bar{B} \quad \left[\text{where } A\bar{A} = B\bar{B} = 0 \right]$$

$$Y = 0 + 0$$

$$\boxed{Y = 0}$$

$$\therefore \boxed{Y = \overline{AB + \bar{A} + AB} = 0} \quad \checkmark$$

Q. find the complement of $AB \cdot (\bar{B}C + AC)$

Ans $\overline{AB \cdot (\bar{B}C + AC)}$

$$\Rightarrow \bar{A}\bar{B} + \overline{(\bar{B}C + AC)}$$

$$\Rightarrow (\bar{A} + \bar{B}) + \overline{(\bar{B}C) \cdot (AC)}$$

$$(\bar{A} + \bar{B}) + \overline{(\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{C})}$$

$$\underline{\underline{\bar{A} + \bar{B} + (B + C) \cdot (\bar{A} + \bar{C})}}$$

Ans

Q. $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}B\bar{C}$

As $\bar{A}\bar{C}(\bar{B}+B) + \bar{A}B\bar{C} \quad [\because B+\bar{B}=1]$

$\bar{A}\bar{C} + \bar{A}B\bar{C}$

$\bar{A}\bar{C}[1+B] \quad [\because 1+B=1]$

$= \underline{\bar{A}\bar{C}}$ As

Q. Reduce the expression, $A+B(\bar{C}+DE)$

As $A+B(\bar{C}+DE)$

$= A+B(\bar{C} \cdot \overline{DE})$

$= A+B(C \cdot \overline{DE}) \quad [\text{De-Morgan's Theorem}]$

$= A+B[C(\bar{D}+\bar{E})] \quad [\text{De-Morgan's Theorem}]$

$= A+B[C\bar{D}+C\bar{E}]$

$= \underline{A+B\bar{C}\bar{D}+B\bar{C}\bar{E}}$

Q. Find the minterm of $A\bar{B}\bar{C}D$

Ans \rightarrow convert $A\bar{B}\bar{C}D$ to binary

$$\rightarrow A\bar{B}\bar{C}D \Rightarrow (1001) \rightarrow (9)_{10}$$

So, its minterm is m_9 Ans

Q. Complement of Boolean algebra expression $AB(BC+AC)$ is

Ans

$$\overline{AB(BC+AC)} \Rightarrow \overline{AB} + \overline{(BC+AC)}$$

$$(\overline{AB}) + (\overline{BC} \cdot \overline{AC})$$

$$(\overline{AB}) + [\overline{(B+C)} \cdot \overline{(A+C)}]$$

$$\overline{AB} + [\overline{B}\overline{A} + \overline{B}\overline{C} + \overline{C}\overline{A} + \overline{C}\overline{C}]$$

$$(\overline{A} + \overline{B}) + [\overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}\overline{C} + \overline{C}\overline{C}] \quad [\because \overline{C}\overline{C} = \overline{C}]$$

$$[\overline{A} + \overline{B} + \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}\overline{C} + \overline{C}]$$

$$\overline{A} + \overline{B} + \overline{A}\overline{B} + \overline{B}\overline{C} + [\overline{A} + 1]\overline{C} \quad \left[\text{where } \overline{A} + 1 = 1 \right]$$

$$\Rightarrow \overline{A} + \overline{B} + \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{C}$$

$$[\overline{A} + \overline{A}\overline{B}] + [\overline{B} + \overline{B}\overline{C}] + \overline{C} \Rightarrow \overline{A}(1 + \overline{B}) + \overline{B}(1 + \overline{C}) + \overline{C}$$

$$\Rightarrow \overline{A} + \overline{B} + \overline{C} \quad \left[\because \text{where } (1 + \overline{B} = 1, 1 + \overline{C} = 1) \right]$$

Q. Simplify $Y = \overline{AB + \bar{A} + AB}$

Ans $Y = (\overline{AB}) \cdot (\bar{\bar{A}}) \cdot (\overline{AB})$

$$Y = AB \cdot A \cdot (\bar{A} + \bar{B})$$

$$Y = ABA \cdot (\bar{A} + \bar{B})$$

$$[\because AA = A]$$

$$Y = AAB \cdot (\bar{A} + \bar{B})$$

$$Y = (AB)(\bar{A} + \bar{B}) \Rightarrow AB\bar{A} + AB\bar{B}$$

$$Y = A\bar{A}B + AB\bar{B} \quad \left[\text{where } A\bar{A} = B\bar{B} = 0 \right]$$

$$Y = 0 + 0$$

$$\boxed{Y = 0}$$

$$\therefore \boxed{Y = \overline{AB + \bar{A} + AB} = 0} \quad \checkmark$$

Q. find the complement of $AB \cdot (\bar{B}C + AC)$

Ans $\overline{AB \cdot (\bar{B}C + AC)}$

$$\Rightarrow \bar{A}\bar{B} + \overline{(\bar{B}C + AC)}$$

$$\Rightarrow (\bar{A} + \bar{B}) + \overline{(\bar{B}C) \cdot (AC)}$$

$$(\bar{A} + \bar{B}) + \overline{(\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{C})}$$

$$\underline{\underline{\bar{A} + \bar{B} + (B + C) \cdot (\bar{A} + \bar{C})}}$$

Ans

Q. Prove two following Identities using Boolean Algebra

(2.10)

$$\overline{A(\overline{A+B})} \cdot \overline{B(\overline{A+B})} = A \oplus B$$

$$\overline{A(\overline{A+B})} + \overline{B(\overline{A+B})} \quad [\because \overline{\overline{A}} = A]$$

$$A[\overline{A+B}] + B[\overline{A+B}]$$

$$[\overline{A+B}][A+B] \Rightarrow [\overline{A+B}][A+B]$$

$$= \overline{A}A + \overline{A}B + \overline{B}A + \overline{B}B$$

$$= \overline{A}B + A\overline{B}$$

$$= \underline{A \oplus B}$$


Q. Draw a logic circuit for the function

$$Y = B \cdot (\overline{A+C}) + \overline{A} \cdot \overline{B}$$

$$Y = \underline{B \cdot \overline{A} + B \cdot \overline{C} + \overline{A} \cdot \overline{B}} \Rightarrow \underline{\overline{A}(B+\overline{B}) + B \cdot \overline{C}}$$

$$\boxed{Y = \overline{A} + B \cdot \overline{C}}$$

Logic circuit is

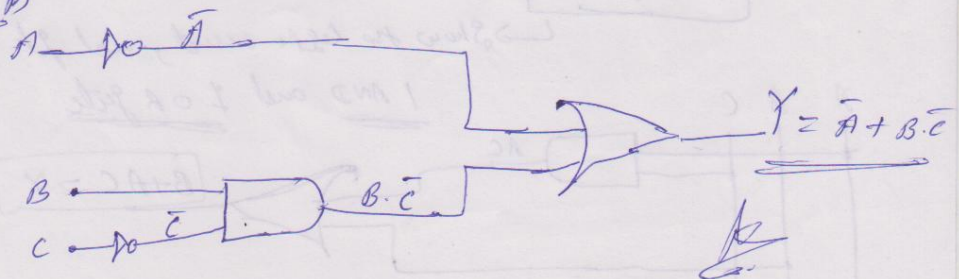


Q.19 Draw a logic circuit to implement the function

$$Y = AB + A(B+C) + B(B+C)$$

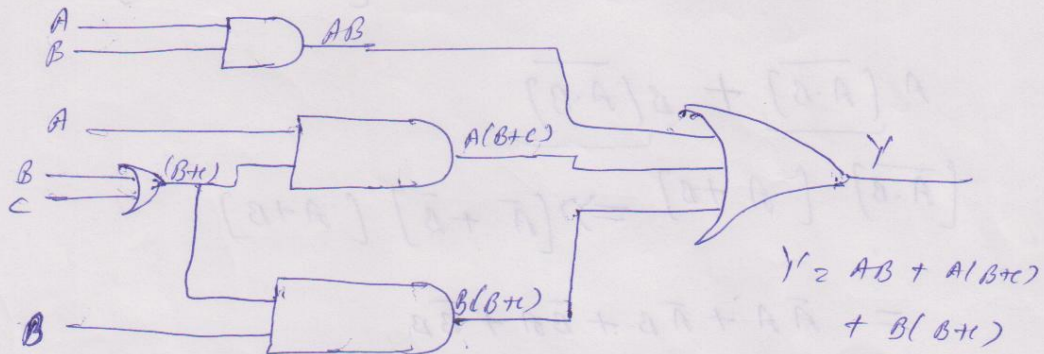(b) Simplify the function and draw logic circuit for the simplified function

Ans (a) It requires 3 AND gate and 2 OR gates



(b) $Y = AB + A(B+C) + B(B+C)$

$$Y = AB + AB + AC + BB + BC$$

$$= AB + AC + B + BC$$

$$= AB + AC + B(1+C)$$

$$= AB + AC + B \cdot 1$$

$$= (A+1)B + AC$$

$$= B + AC$$


$$\left[\begin{array}{l} \because AB + AB = AB \\ B \cdot B = B \end{array} \right]$$

$$\left[\because 1+C = 1 \right]$$

$$\left[\because A+1 = 1 \right]$$

$$Y = B + AC$$

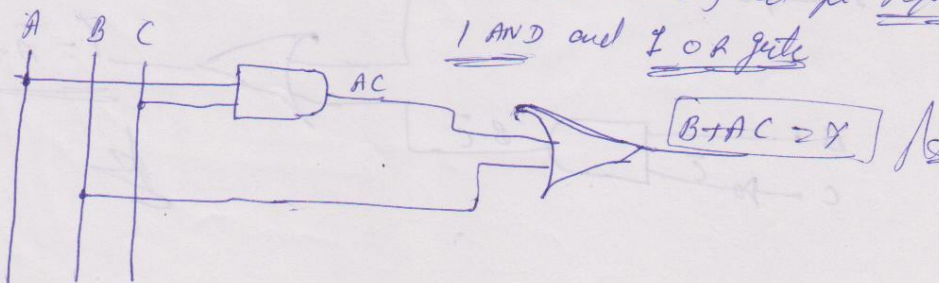→ Show the logic circuit, and it requires 1 AND and 1 OR gate




Q. (a) Draw a logic circuit for the boolean expression

$$Y = AB + AC + BD + CD$$

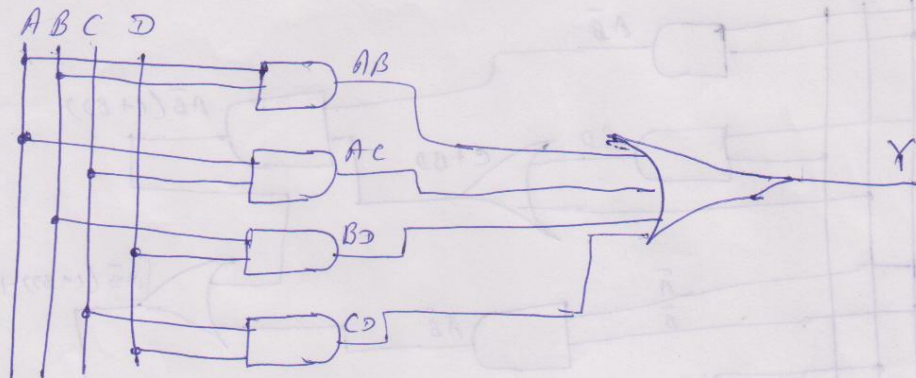(b) Simplify the expression and draw logic circuit for the simplified expression.

Ans (a) It required 4 AND gate and one OR gate



(b)


$$Y = AB + AC + BD + CD$$

$$Y = A(B+C) + D(B+C)$$

$$Y = (A+D)(B+C)$$

It requires 2 OR and 1 AND gates

A B C D

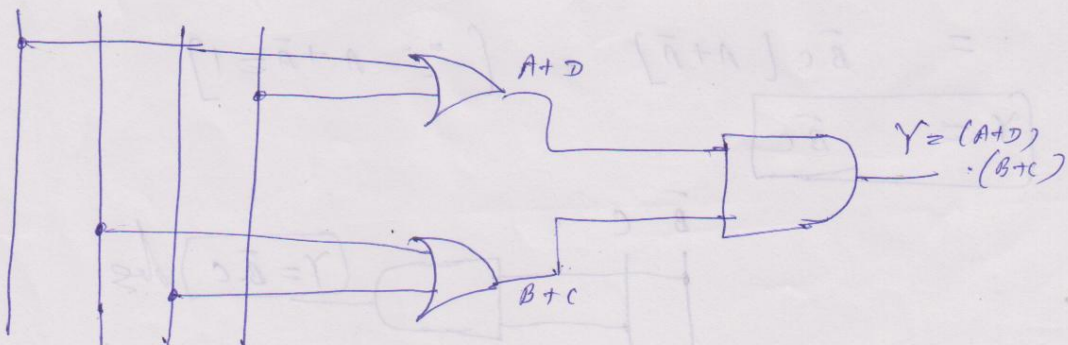


Q- (a) Draw logic circuit for the expression

$$Y = [A\bar{B}(C+BD) + \bar{A}\bar{B}]C$$

(b) Simplify the expression and draw logic for the simplified expression.

Ans

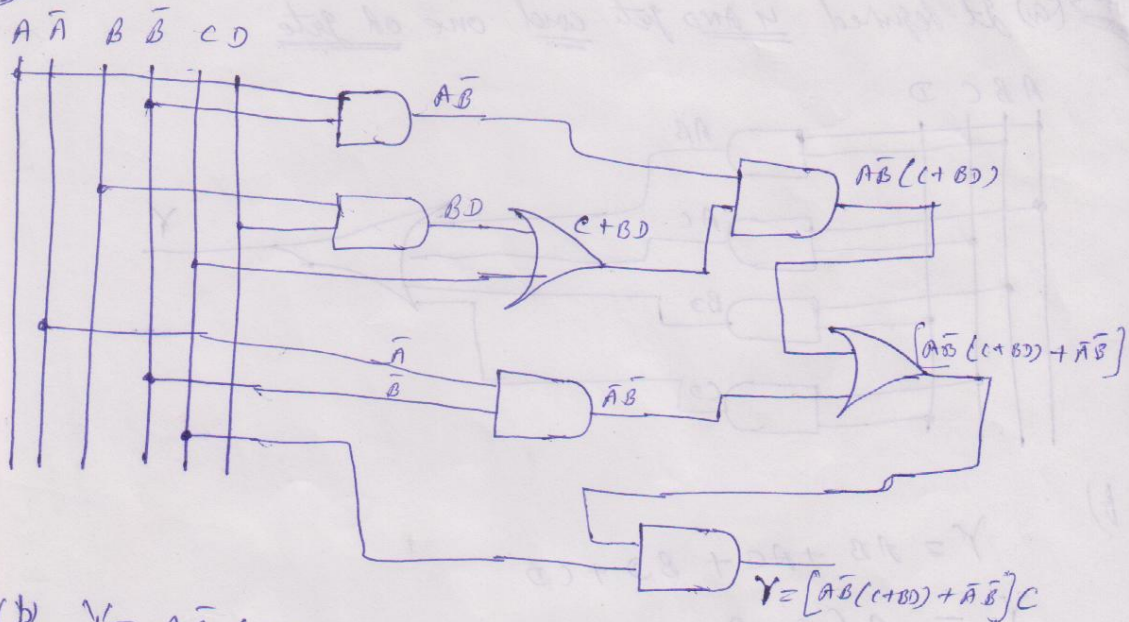

(b) $Y = A\bar{B}(C+BD) + \bar{A}\bar{B}]C$

$$= (A\bar{B}C + A\bar{B}BD + \bar{A}\bar{B})C$$

$$[\because B\bar{B} = 0]$$

$$= (A\bar{B}C + 0 + \bar{A}\bar{B})C$$

$$= A\bar{B}CC + \bar{A}\bar{B}C$$

$$[\because CC = C]$$

$$= A\bar{B}C + \bar{A}\bar{B}C$$

$$= \bar{B}C[A + \bar{A}]$$

$$[\because A + \bar{A} = 1]$$

$$Y = \bar{B}C$$

