
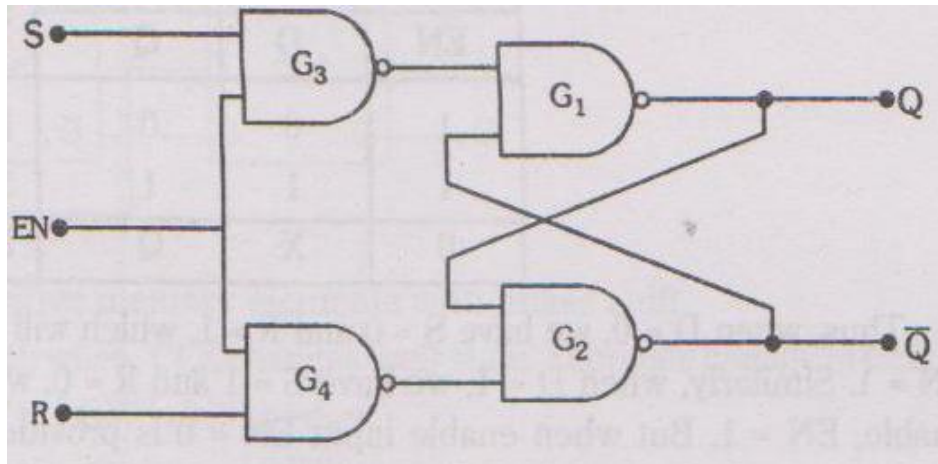


# Gated latches(Clocked Flip Flop)
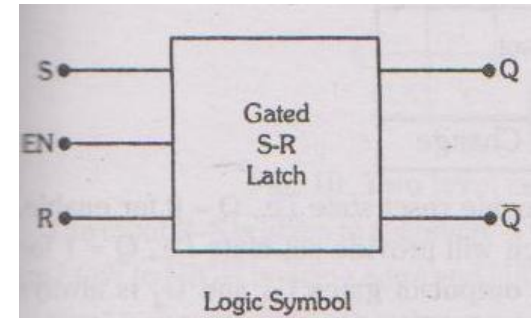
## S-R Latch with control input

$C = 0$  disables all latch state changes

Control signal **enables** data change when  $C = 1$



$C$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table

## Case I : when $S = 0$ , $R = 0$

Output of gates **G3** and **g4** are always '1' irrespective of clock signal


Thus '1' is input to gates **G1** and **g2** which provides the output for no change

Inputs		Output	State
S	R	Q	
0	0	X	Invalid
0	1	0	Reset
1	0	1	Set
1	1	Q	No Change
 
## Case II : when $S = 0$ , $R = 1$

Output of gates **G3** is always '1' and **g4** is always '0' irrespective of clock signal


Thus the is input to gates **G1** and **g2** are '1' and '0' respectively


 
### Case III : when $S = 1$ , $R = 0$

Output of gates **G3** is always '0' and **G4** is always '1' irrespective of clock signal

Thus the is input to gates **G1** and **G2** are '0' and '1' respectively



### Case IV : when $S = 1$ , $R = 1$

Output of gates **G3** and **G4** are always '0' irrespective of clock signal

Thus the is input to gates **G1** and **G2** are '0' respectively

Inputs			Output	State
Clk	S	R	Q	
↑	0	0	Q	No Change
↑	0	1	0	Reset
↑	1	0	1	Set
↑	1	1	X	Invalid
0	X	X	Q	No Change
1	X	X	Q	No Change
↓	X	X	Q	No Change

Positive Edge Triggered Clock

Flip-flop is disabled