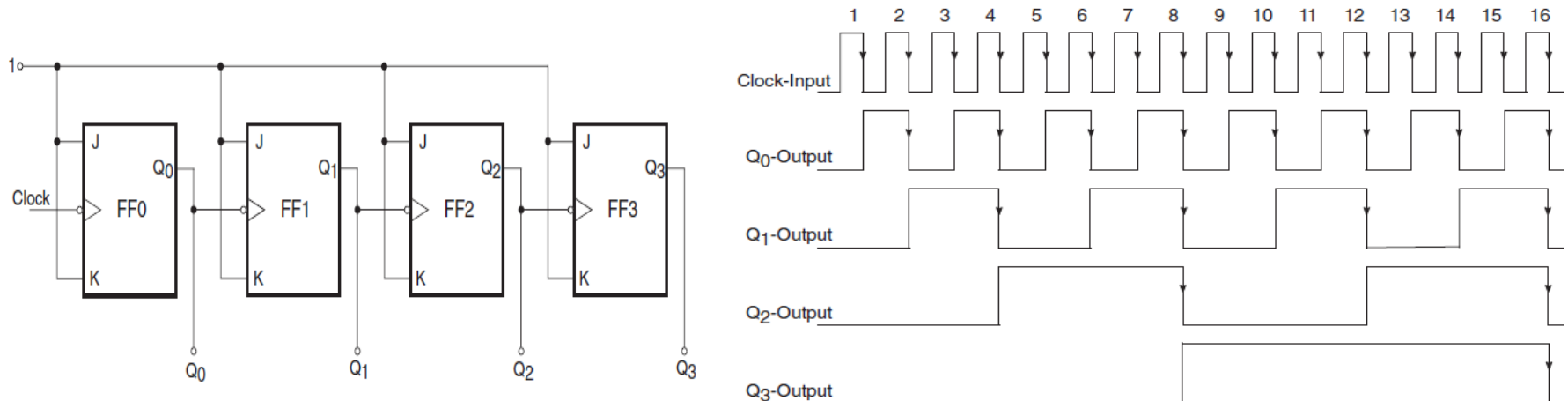


Modulus of a Counter


Binary Ripple Counter – Operational Basics

- The operation of a binary ripple counter can be best explained with the help of a typical counter of this type.
- Figure shows a four-bit ripple counter implemented with negative edge-triggered J-K flip-flops wired as toggle flip-flops.
- The output of the first flip-flop feeds the clock input of the second, and the output of the second flip-flop feeds the clock input of the third, the output of which in turn feeds the clock input of the fourth flip-flop.
- The outputs of the four flip-flops are designated as Q0 (LSB flip-flop), Q1, Q2 and Q3 (MSB flip-flop).




UP/DOWN Counters



- Counters are also available in integrated circuit form as UP/DOWN counters, which can be made to operate as either UP or DOWN counters.
- UP counter is one that counts upwards or in the forward direction by one LSB every time it is clocked.
- A four-bit binary UP counter will count as 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1101, 1110, 1111, 0000, 0001, and so on.
- DOWN counter counts in the reverse direction or downwards by one LSB every time it is clocked. The four-bit binary DOWN counter will count as 0000, 1111, 1110, 1101, 1100, 1011, 1010, 1001, 1000, 0111, 0110, 0101, 0100, 0011, 0010, 0001, 0000, 1111

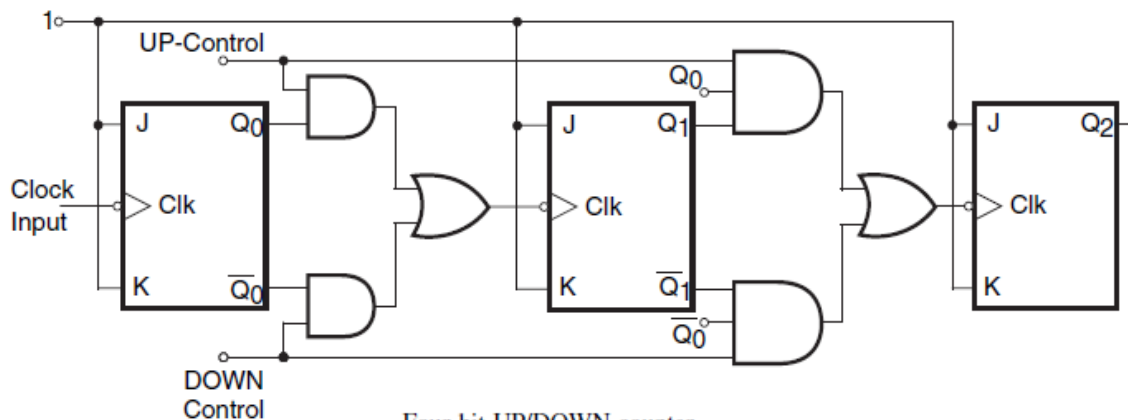

- shows a three-bit binary UP/DOWN counter. This is only one possible logic arrangement. As we can see, the counter counts upwards when UP control is logic '1' and DOWN Control is logic '0'.
- In this case the clock input of each flip-flop other than the LSB flip-flop is fed from the normal output of the immediately preceding flip-flop. The counter counts downwards when the UP control input is logic '0' and DOWN control is logic '1'.

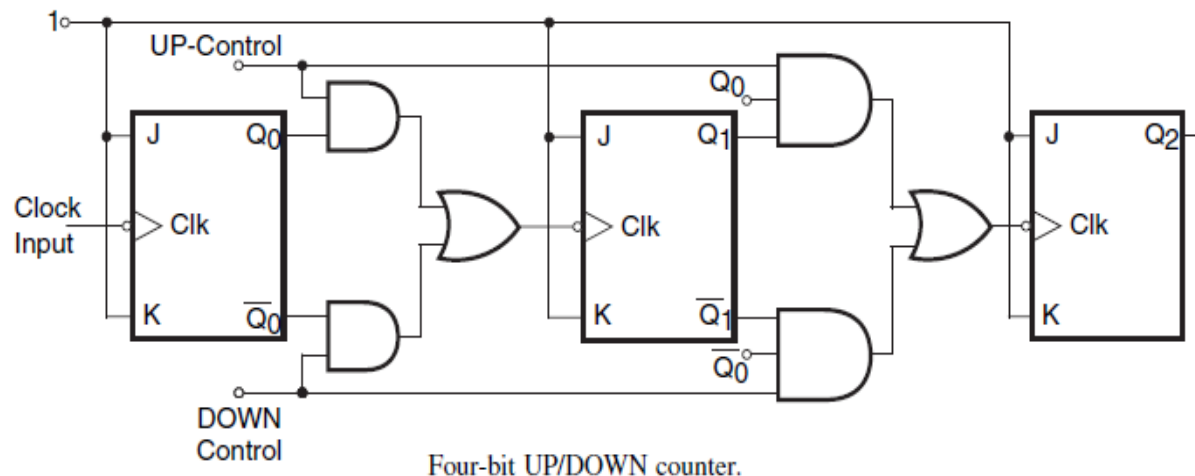

BCD Counter: State Diagram

  

Qn	Qn+1		J	K
0	0		0	X
0	1		1	X
1	0		X	1
1	1		X	0

Table 11.12 Example 11.9.

Present state			Next state			Inputs					
C	B	A	C	B	A	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	1	0	0	X	1	X	0	X
0	0	1	0	0	0	0	X	0	X	X	1
0	1	0	1	0	1	1	X	X	1	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	0	0	0	X	1	X	1	X	1

Solution

- The number of flip-flops required is three.
- Table 11.12 shows the desired circuit excitation table.
- The Karnaugh maps for J_A , K_A , J_B , K_B , J_C and K_C are shown in Figs 11.30(a) to (f) respectively.
- The simplified Boolean expressions are as follows:

$$J_A = B.\overline{C}$$

$$K_A = 1$$

	\overline{A}	A
$\overline{C}\overline{B}$		X
$\overline{C}B$	1	X
CB		X
$C\overline{B}$		X

(a)

	\overline{A}	A
$\overline{C}\overline{B}$	X	1
$\overline{C}B$	X	1
CB	X	1
$C\overline{B}$	X	1


(b)

$$J_B = A.C + \overline{A}.\overline{C}$$

	\overline{A}	A
$\overline{C}\overline{B}$	1	
$\overline{C}B$	X	X
CB	X	X
$C\overline{B}$		1

(c)

Example

 

Q _n	Q _n +1		J	K
0	0		0	X
0	1		1	X
1	0		X	1
1	1		X	0

P.S				N.S										
Q2	Q1	Q0		Q2	Q1	Q0	JQ2	KQ2	JQ1	KQ1	JQ0	KQ0		
0	0	1		0	1	0	0	x	1	x	x	1		
0	1	0		1	0	1	1	x	x	1	1	x		
1	0	1		1	1	1	x	0	1	x	x	0		
1	1	1		0	0	1	x	1	x	1	x	0		

P.S				N.S								
Q2	Q1	Q0		Q2	Q1	Q0	J _{Q2}	K _{Q2}	J _{Q1}	K _{Q1}	J _{Q0}	K _{Q0}
0	0	1		0	1	0	0	x	1	x	x	1
0	1	0		1	0	1	1	x	x	1	1	x
1	0	1		1	1	1	x	0	1	x	x	0
1	1	1		0	0	1	x	1	x	1	x	0

Step 4: drawn the K map

For J_{Q2} and K_{Q2}

Q2	Q1Q0			
	00	01	11	10
0				
1				

For J₂ = Q₁

Q2	Q1Q0			
	00	01	11	10
0				
1				

For K₂ = Q₁

For J_{Q1} and K_{Q1}

Q2	Q1Q0			
	00	01	11	10
0				
1				

For J₁ = 1

Q2	Q1Q0			
	00	01	11	10
0				
1				

For K₁ = 1

For J_{Q0} and K_{Q0}

Q2	Q1Q0			
	00	01	11	10
0				
1				

For J₀ = 1

Q2	Q1Q0			
	00	01	11	10
0				
1				

For K₀ = Q'₂

Step 5

$$J_0 = 1, \quad K_0 = Q_2'$$

$$J_1 = 1, \quad K_1 = 1$$

$$J_2 = Q_1, \quad K_2 = Q_1$$

Step 6: draw the circuit diagram