

DON't Care condition

- In few logic circuits, output is not given or specified for certain combination of input.
- In such case output level is not defined, it can 'high' or 'low' either '1' or '0'
- These output are denoted are 'd' or 'x' or 'Φ'

Example:

Minimize the flowing function using K – map. Right truth table and implementing the circuit .

$$f(A,B,C,D,E) = \sum m(2,4,5,13,15) + \sum d(8,9,10,11)$$

CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
AB	0	0	1	1
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	1	0
$A\bar{B}$	x	x	x	x

CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
AB	0	0	1	1
$\bar{A}\bar{B}$	1	1	0	0
$\bar{A}B$	0	1	1	0
$A\bar{B}$	0	1	1	1

- Example:

Minimize the flowing function using K – map. Right truth table and implementing the circuit using NAND gate only.

$$f(A, B, C, D, E) = \sum m(2, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$$

Minimization of product of Sum from using K map

Decimal Number	Variables			Maxterms	Maxterm Designation
	A	B	C		
0	0	0	0	$A + B + C$	M_0
1	0	0	1	$A + B + \bar{C}$	M_1
2	0	1	0	$A + \bar{B} + C$	M_2
3	0	1	1	$A + \bar{B} + \bar{C}$	M_3
4	1	0	0	$\bar{A} + B + C$	M_4
5	1	0	1	$\bar{A} + B + \bar{C}$	M_5
6	1	1	0	$\bar{A} + \bar{B} + C$	M_6
7	1	1	1	$\bar{A} + \bar{B} + \bar{C}$	M_7