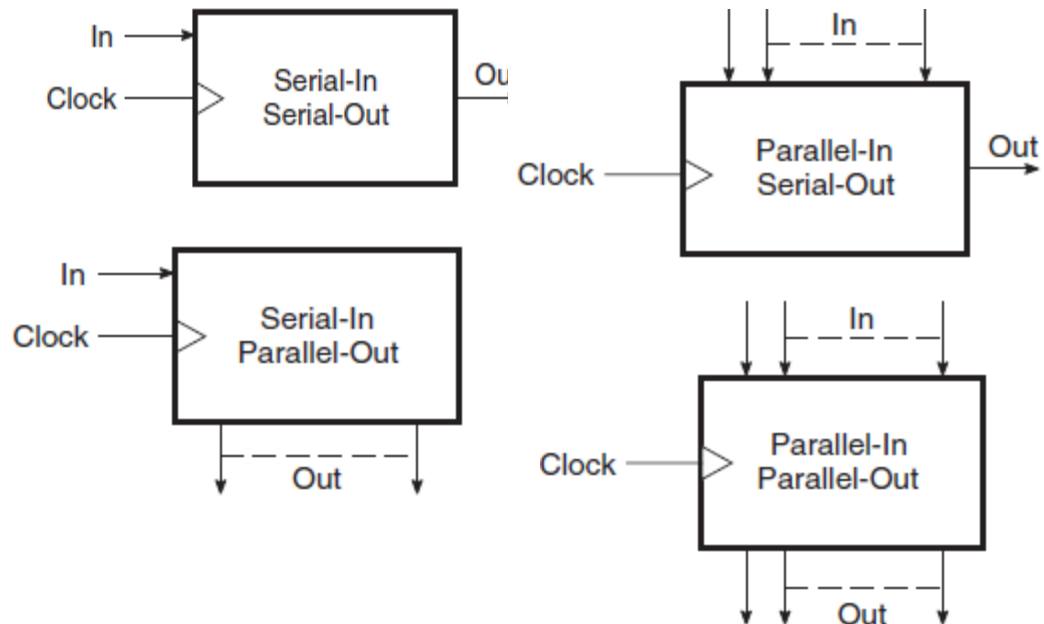




# Shift Registers

- Shift register can store data as well as shift data .
  - The storage capacity of a shift register equals the total number of bits of digital data it can store , which in turn depends upon the number of flip-flops used to construct the shift register
- 
- Basic types of shift registers
  - serial-in serial-out (SISO)
  - serial-in parallel-out (SIPO)
  - parallel-in serial-out (PISO)
  - parallel-in parallel-out (PIPO)



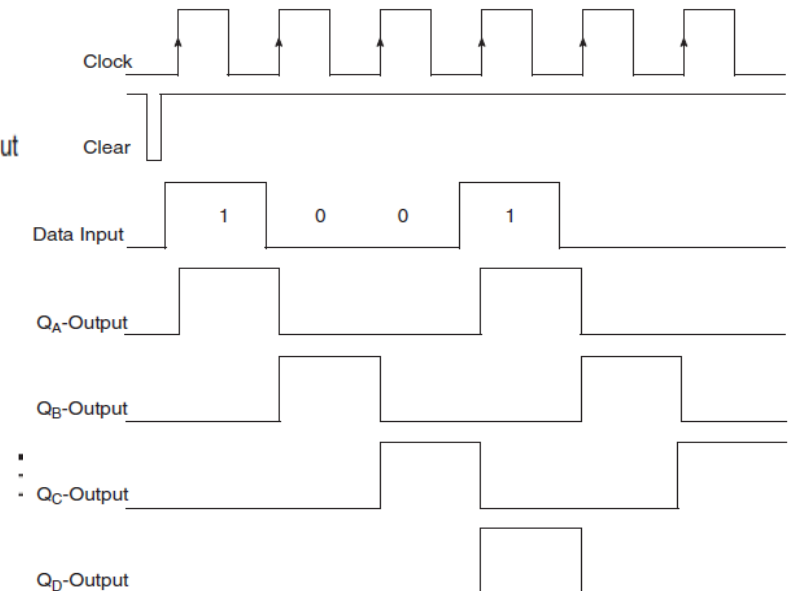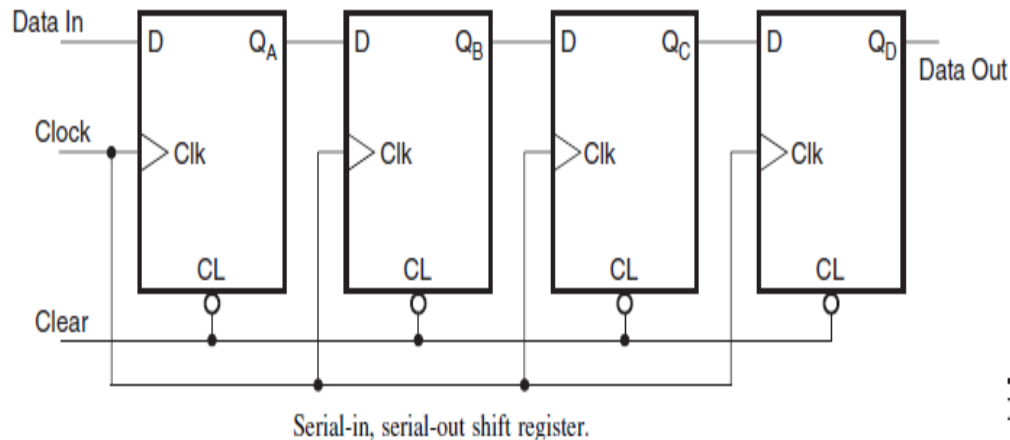
# Serial-In Serial-Out Shift Register

- The basic four-bit serial-in serial-out shift register implemented using D flip-flops
- The circuit functions as follows.
  - A reset applied to the CLEAR input of all the flip-flops resets their Q outputs to 0s.
  - During the first clock transition, the QA output goes from logic '0' to logic '1'.



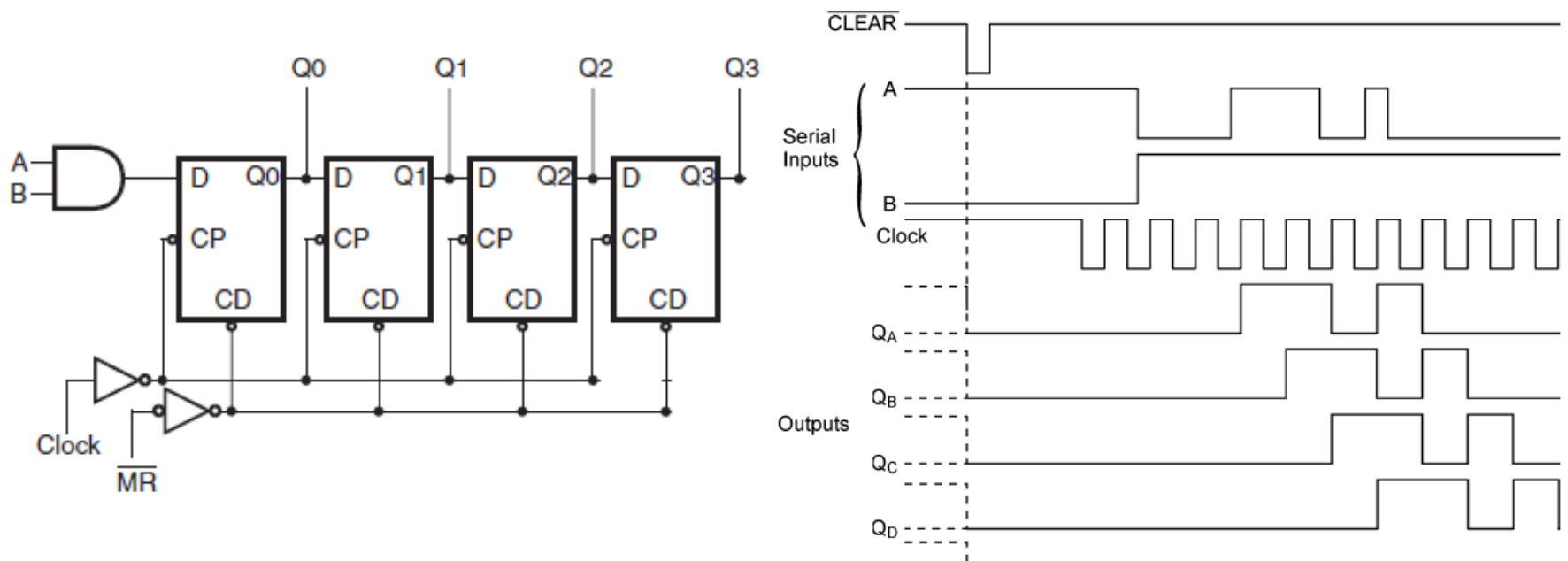
# *Serial-In Parallel-Out Shift Register*

- A serial-in parallel-out shift register is architecturally identical to a serial-in serial-out shift register
- except that in the case of the former all flip-flop outputs are also brought out on the IC terminals



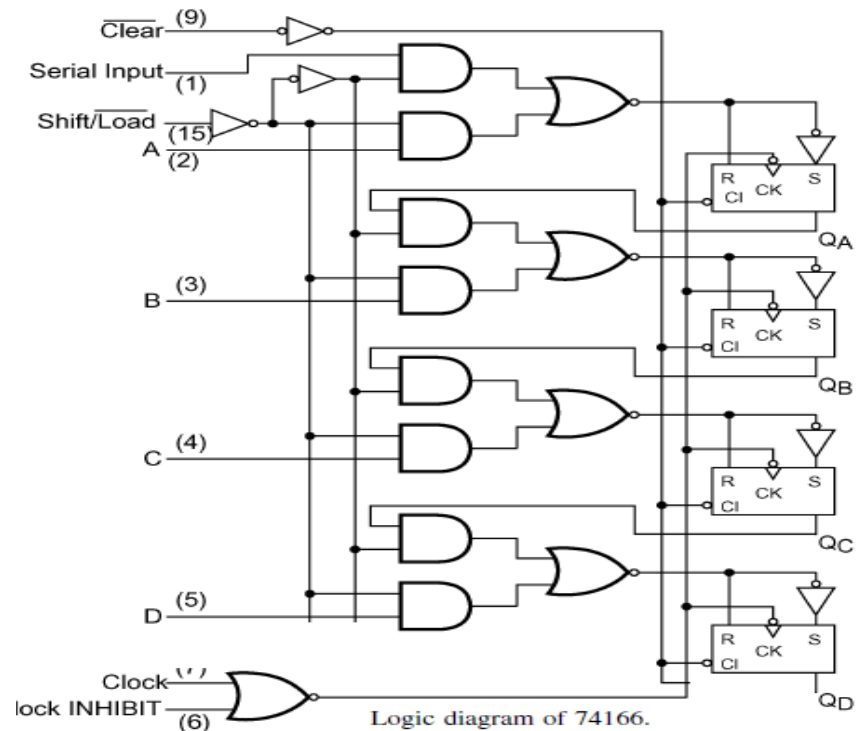
# *Parallel-In Serial-Out Shift Register*

- A logic diagram is that of IC 74166, which is an eight-bit parallel/serial-in, serial-out shift register belonging to the TTL family of devices.
- The parallel-in or serial-in modes are controlled by a SHIFT/LOAD input.


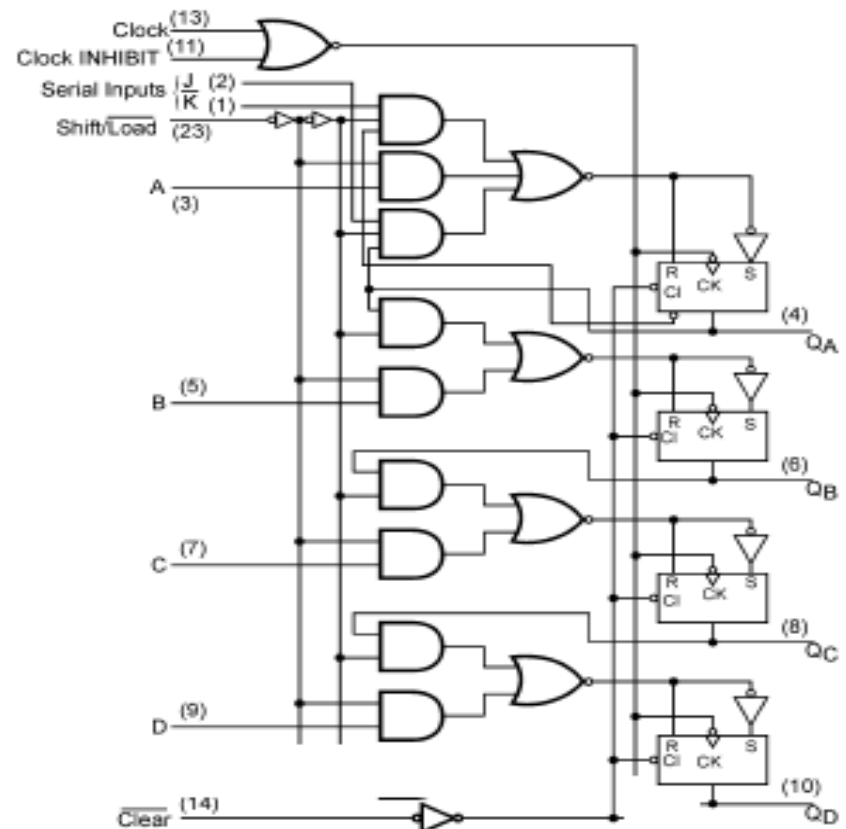
# *Parallel-In Parallel-Out Shift Register*

- hardware of a parallel-in parallel-out shift register is similar to that of a parallel-in serial-out shift register
- The parallel-in or serial-in modes are controlled by a SHIFT/LOAD input.



Logic diagram of IC 74195