

# OR Operator

- Another basic operator is the OR

- Consider:

If I have *cash* OR *a credit card*,  
then *I can pay the bill*

- OR works such that the output is *true*,  
if either of the two inputs is *true*

OR Operator  
Truth Table

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1