

Encoders

- An *encoder* is a multiplexer without its single output line
- It is a combinational logic function that has 2^n (or fewer) input lines and n output lines,
- The n output lines generate the binary code for the possible 2^n input lines.
- Let us take the case of an octal-to-binary encoder. Such an encoder would have eight input lines,


 


Table 8.8 Truth table of an encoder.


D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

Types of Encoder

- Octal to binary Encoder
- Decimal to BCD Encoder
- Priority Encoder

Octal to binary Encoder

 

$$B_2 = O_4 + O_5 + O_6 + O_7$$

$$B_1 = O_2 + O_3 + O_6 + O_7$$


$$B_0 = O_1 + O_3 + O_5 + O_7$$

Inputs Octal Digits	Decimal Equivalent	Outputs		
		Binary Bits		
		B_2	B_1	B_0
O_0	0	0	0	0
O_1	1	0	0	1
O_2	2	0	1	0
O_3	3	0	1	1
O_4	4	1	0	0
O_5	5	1	0	1
O_6	6	1	1	0
O_7	7	1	1	1

$$B_2 = O_4 + O_5 + O_6 + O_7$$

$$B_1 = O_2 + O_3 + O_6 + O_7$$


$$B_0 = O_1 + O_3 + O_5 + O_7$$

 


8-to-3 Binary Encoder

At any one time, only one input line has a value of 1.

Inputs								Outputs		
I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	y_2	y_1	y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

Decimal to BCD Encoder

 

Decimal	Binary	BCD			
		A	B	C	D
0	0000 0000	0	0	0	0
1	0000 0001	0	0	0	1
2	0000 0010	0	0	1	0
3	0000 0011	0	0	1	1
4	0000 0100	0	1	0	0
5	0000 0101	0	1	0	1
6	0000 0110	0	1	1	0
7	0000 0111	0	1	1	1
8	0000 1000	1	0	0	0
9	0000 1001	1	0	0	1

8-to-3 Priority Encoder

- What if more than one input line has a value of 1?
- Ignore “lower priority” inputs.
- **Idle** indicates that no input is a 1.
- Note that polarity of **Idle** is opposite from Table 4-8 in Mano

Inputs								Outputs			Idle
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀	
0	0	0	0	0	0	0	0	x	x	x	1
1	0	0	0	0	0	0	0	0	0	0	0
X	1	0	0	0	0	0	0	0	0	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	X	X	1	0	1	1	0	0
X	X	X	X	X	X	X	1	1	1	1	0

Priority Encoder (8 to 3 encoder)

- Assign priorities to the inputs
- When more than one input are asserted, the output generates the code of the input with the highest priority

- Priority Encoder :

$H7=I7$ (Highest Priority)

$H6=I6.I7'$

$H5=I5.I6'.I7'$

$H4=I4.I5'.I6'.I7'$

$H3=I3.I4'.I5'.I6'.I7'$

$H2=I2.I3'.I4'.I5'.I6'.I7'$

$H1=I1.I2'.I3'.I4'.I5'.I6'.I7'$

$H0=I0.I1'.I2'.I3'.I4'.I5'.I6'.I7'$


$IDLE= I0'.I1'.I2'.I3'.I4'.I5'.I6'.I7'$

- Encoder

$Y0 = I1 + I3 + I5 + I7$


$Y1 = I2 + I3 + I6 + I7$

$Y2 = I4 + I5 + I6 + I7$

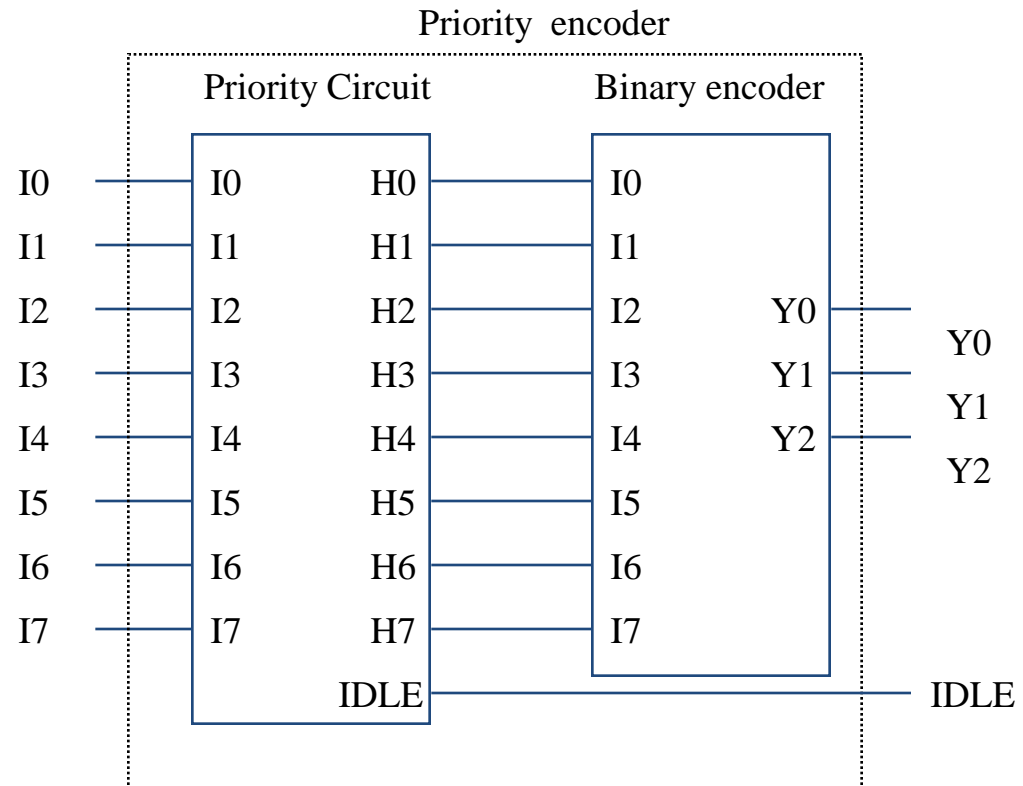

Binary Decoder

 - Black box with n input lines and 2^n output lines
- Only one output is a 1 for any given input





2-to-4 Binary Decoder

Truth Table:

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 
 
- From truth table, circuit for 2x4 decoder is:
- Note: Each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' or XY)



3-to-8 Binary Decoder

Truth Table:

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

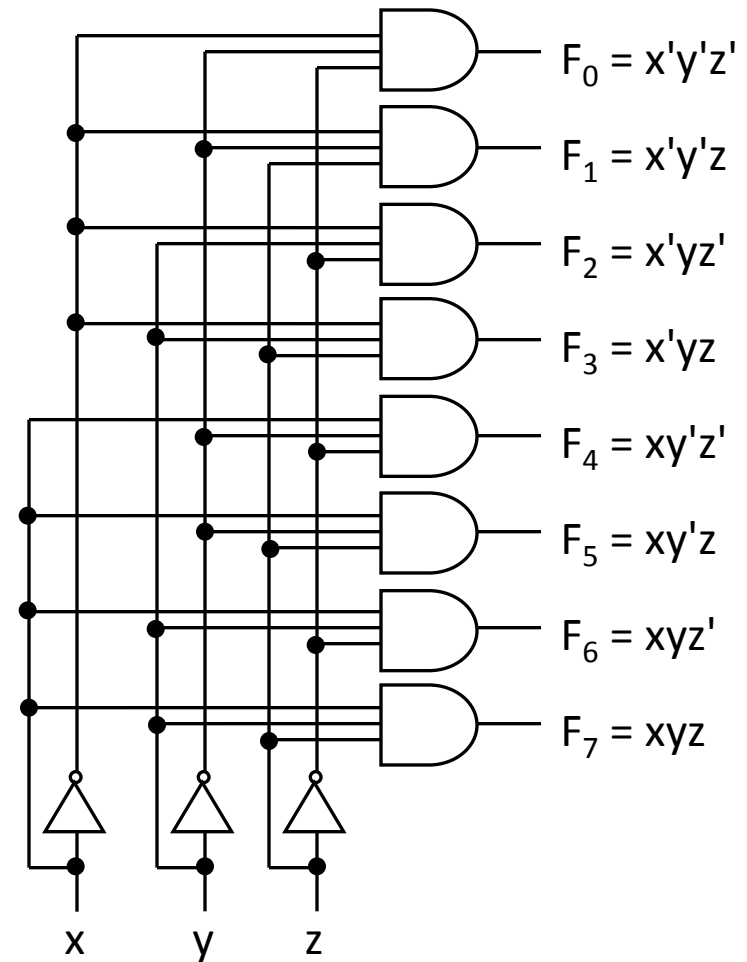 

Implementing Functions Using Decoders

- Any n -variable logic function can be implemented using a single n -to- 2^n decoder to generate the minterms
 - OR gate forms the sum.
 - The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.
- Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder with m OR gates.
- Suitable when a circuit has many outputs, and each output function is expressed with few minterms.


Implementing Functions Using Decoders

- Example: Full adder

$$S(x, y, z) = \Sigma (1, 2, 4, 7)$$


$$C(x, y, z) = \Sigma (3, 5, 6, 7)$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Standard MSI Binary Decoders Example

74138 (3-to-8 decoder)

 

(a)

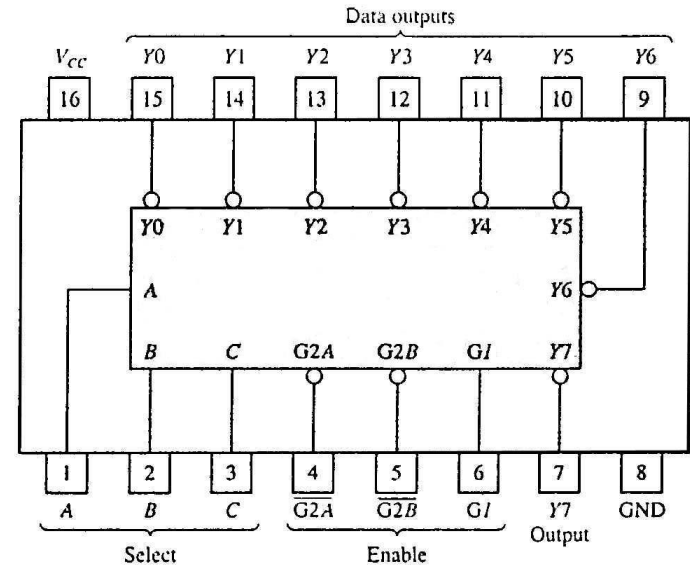

(b)

Inputs					Outputs							
Enable		Select										
G1	$\overline{G2}^*$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	L	H	H	H	H	H	H	L	H	H
H	L	H	H	L	H	H	H	H	H	H	L	H
H	L	H	H	H	H	H	H	H	H	H	H	L
x	H	x	x	x	H	H	H	H	H	H	H	H
L	x	x	x	x	H	H	H	H	H	H	H	H

$$\overline{G2}^* = \overline{G2A} + \overline{G2B}$$

(c)

(a) Logic circuit.

(b) Package pin configuration.

(c) Function table.