

Implementing Combinational Logic

- The different steps involved in the design of a combinational logic circuit are as follows:
 1. Statement of the problem.
 2. Identification of input and output variables.
 3. Expressing the relationship between the input and output variables.
 4. Construction of a truth table to meet input–output requirements.
 5. Writing Boolean expressions for various output variables in terms of input variables.
 6. Minimization of Boolean expressions.
 7. Implementation of minimized Boolean expressions.