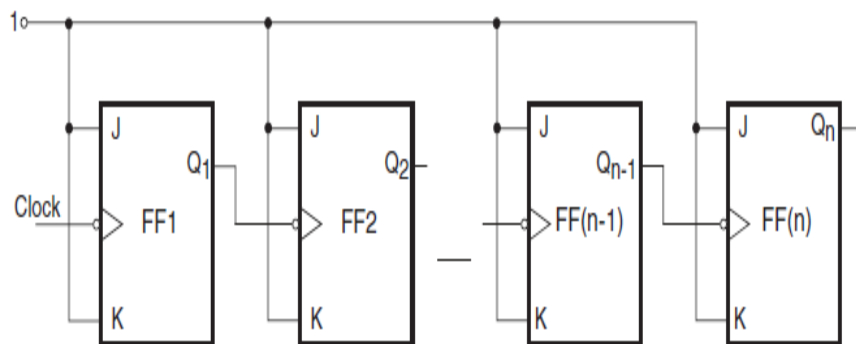


# Ripple (Asynchronous) Counter

- A ripple counter is a cascaded arrangement of flip-flops where the output of one flip-flop drives the clock input of the following flip-flop.
- In a ripple counter, also called an *asynchronous counter* or a *serial counter*
- The clock input is applied only to the first flip-flop, also called the input flip-flop, in the cascaded arrangement.
- The output of the first flip-flop acts as the clock input to the second flip-flop, the output of the second flip-flop feeds the clock input of the third flip-flop and so on.
- In general, in an arrangement of  $n$  flip-flops, the clock input to the  $n$ th flip-flop comes from the output of the  $(n-1)$ th flip-flop for  $n > 1$ .



Generalized block schematic of  $n$ -bit binary ripple counter.

