

# Introduction Logic Gates And Truth Table

- The most basic **digital devices** are called **gates**.
- Gates got their name from their function of allowing or blocking (gating) the flow of digital information.
- A gate has one or more inputs and produces an output depending on the input(s).
- A gate is called a combinational circuit.

# Types Of Logic Gates

These are the basic gates:

- 1) OR
- 2) AND
- 3) NOT

Some more logics can be made by combining these basic gates.

Universal gates:


- 1) NOR
- 2) NAND

Combinational gates:


- 1) XOR
- 2) XNOR
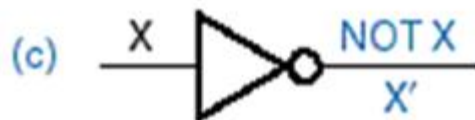
# Digital Logic


- Binary system -- 0 & 1, LOW & HIGH, negated and asserted.
- Basic building blocks -- AND, OR, NOT



X	NOT X
0	1
1	0

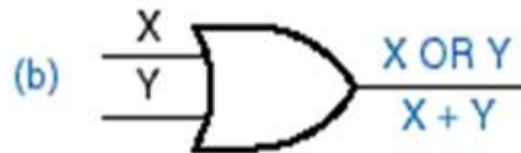

X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

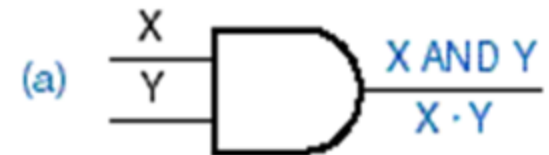

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1