

## CODE - Converters

(D-14)


⇒ are used to convert one type of code into another type of code.

Code converters are various types, such as

- (i) Binary to Gray code converter
- (ii) Gray code to Binary converter
- (iii) BCD To Excess-3 code converter
- (iv) Excess-3 To BCD code converter
- (v) Gray code to Excess-3 code converter
- (vi) BCD To 7-segment code converter / decoder

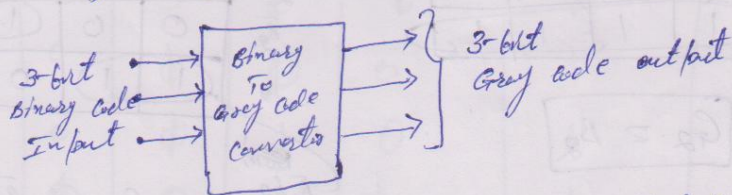
### # Binary To Gray code converter

⇒ for block diagram of 3-bit binary to gray code converter is:



Let the input variable be  $b_2, b_1, b_0$  and output variable be

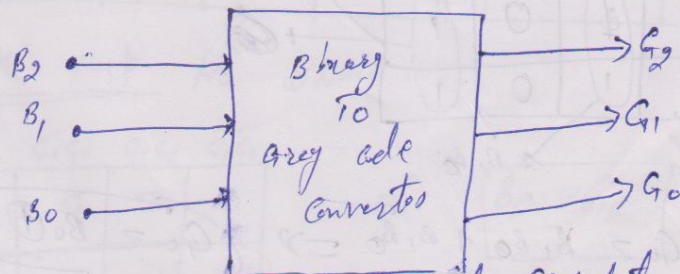$G_2, G_1, G_0$ . Then for block diagram is



Let  $B_2$  be the binary bit and  $G_2$  be gray bit

Decimal equivalent	Binary inputs			Gray output		
	$b_2$	$b_1$	$b_0$	$G_2$	$G_1$	$G_0$
0	0	0	0	0	0	0
1	0	0	1	0	0	1
2	0	1	0	0	1	1
3	0	1	1	0	1	0
4	1	0	0	1	1	0
5	1	0	1	1	1	1
6	1	1	0	1	0	1
7	1	1	1	1	0	0

$\Leftrightarrow$  Minimized logic  $f_n$  using K-map

for  $G_2$

	$b_1 \bar{b}_0$	$\bar{b}_1 \bar{b}_0$	$b_1 b_0$	$\bar{b}_1 b_0$
$b_2$	0	0	0	0
$\bar{b}_2$	1	1	1	1

$$G_2 = b_2$$

for  $G_1$

	$b_1 \bar{b}_0$	$\bar{b}_1 \bar{b}_0$	$b_1 b_0$	$\bar{b}_1 b_0$
$b_2$	0	0	1	1
$\bar{b}_2$	1	1	0	0

$$G_1 = b_2 \bar{b}_0 + \bar{b}_2 b_0$$

$$G_1 = b_2 \oplus b_0$$

$$G_1 = b_1 \oplus b_3$$

for  $G_0$


	$b_1 \bar{b}_0$	$\bar{b}_1 \bar{b}_0$	$b_1 b_0$	$\bar{b}_1 b_0$
$b_2$	0	0	0	1
$\bar{b}_2$	0	1	0	1

$$G_0 = b_1 b_0 + \bar{b}_1 \bar{b}_0 \Rightarrow G_0 = b_0 \oplus b_1$$



## Circuit Implementation using gates

(D-13)

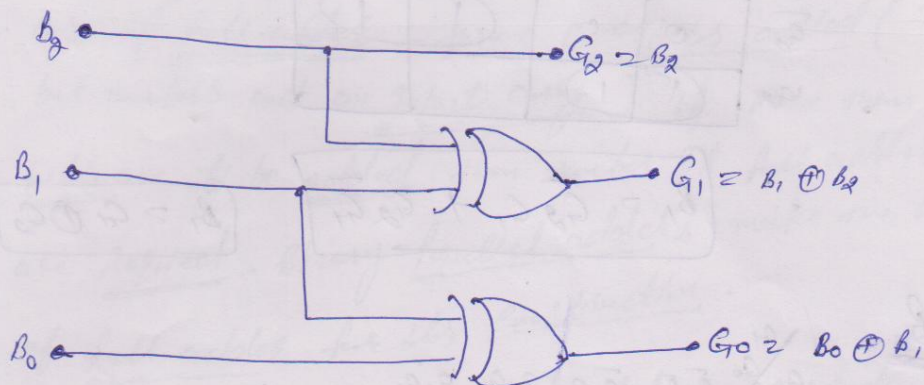

## # 3-bit Gray code to Binary converter

Decimal Equivalent	Gray code			Binary code		
	$G_2$	$G_1$	$G_0$	$B_2$	$B_1$	$B_0$
0	0	0	0	0	0	0
1	0	0	1	0	0	1
2	0	1	0	0	1	0
3	0	1	1	0	1	1
4	1	0	0	1	0	0
5	1	0	1	1	0	1
6	1	1	0	1	1	0
7	1	1	1	1	1	1

$B_0 = G_0$

K-map as shown as

$G_1 \backslash G_0$	$\bar{G}_1 \bar{G}_0$	$\bar{G}_1 G_0$	$G_1 \bar{G}_0$	$G_1 G_0$
$\bar{G}_0$	0	0	0	0
$G_0$	1	1	1	1

$$B_2 = G_2$$

for  $B_1$

$G_1 \backslash G_2 \backslash G_0$	$\bar{G}_1 \bar{G}_0$	$\bar{G}_1 G_0$	$G_1 \bar{G}_0$	$G_1 G_0$
$\bar{G}_2$	0	0	1	1
$G_2$	1	1		

$$B_1 = \bar{G}_2 G_1 + G_2 \bar{G}_1$$

$$B_1 = G_1 \oplus G_2$$

for  $B_0$

$G_1 \backslash G_2 \backslash G_0$	$\bar{G}_1 \bar{G}_0$	$\bar{G}_1 G_0$	$G_1 \bar{G}_0$	$G_1 G_0$
$\bar{G}_2$	0	1	0	1
$G_2$	1	0	1	0

$$B_0 = \bar{G}_2 \bar{G}_1 G_0 + \bar{G}_2 G_1 \bar{G}_0 + G_2 \bar{G}_1 \bar{G}_0 + G_2 G_1 G_0$$

$$B_0 = \bar{G}_2 (\bar{G}_1 G_0 + G_1 \bar{G}_0) + G_2 (\bar{G}_1 \bar{G}_0 + G_1 G_0)$$

$$B_0 = \bar{G}_2 (G_1 \oplus G_0) + G_2 (G_1 \oplus G_0)$$

$$B_0 = \bar{G}_2 (G_1 \oplus G_0) + G_2 (G_1 \oplus G_0)$$

$$B_0 = G_1 \oplus G_0 + G_2$$

Circuit Implementation is as shown  $\Rightarrow$

