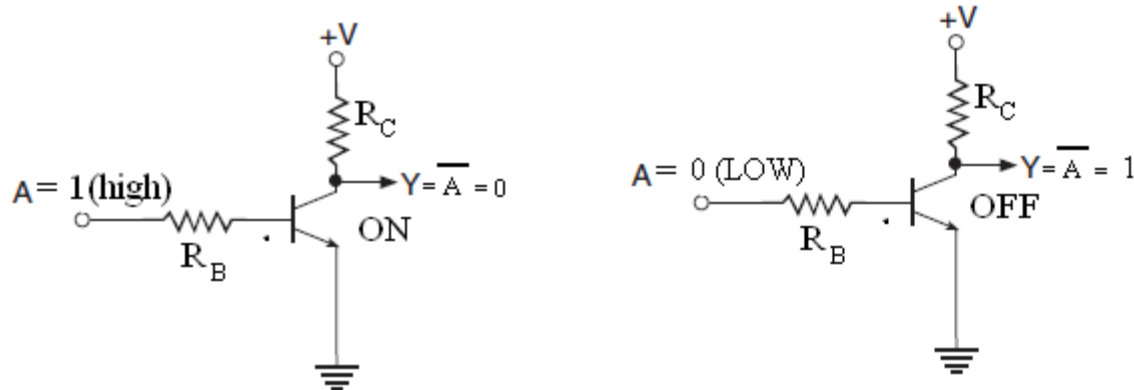


# Resistor Transistor Logic(RTL)

- RTL is the earliest logic family but it has become absolute hour
- Combination of resistor and transistor to designed the logic family
- Invertors (NOT GATE)



# Resistor Transistor Logic(RTL)

- For NOR Gate ;

A	B	O/P
0	0	1
0	1	0
1	0	0
1	1	0

- If  $A = B = 0$  both transistor remain off. the current through  $R_C$  is zero so drop across it is zero. Then output  $Y = 1$
- If  $A = 0$   $B = 1$  Transistor  $Q_1$  is OFF and  $Q_2$  goes to saturation. Then output  $Y = 0$
- If  $A = 1$   $B = 0$  Transistor  $Q_1$  is in saturation and  $Q_2$  is turned off. So the output voltage is  $V_{CE1(sat)}$ . Then output  $Y = 0$
- If  $A = B = 1$  both transistors are in saturation and the output voltage is equal to saturation voltage  $Y = 0$

