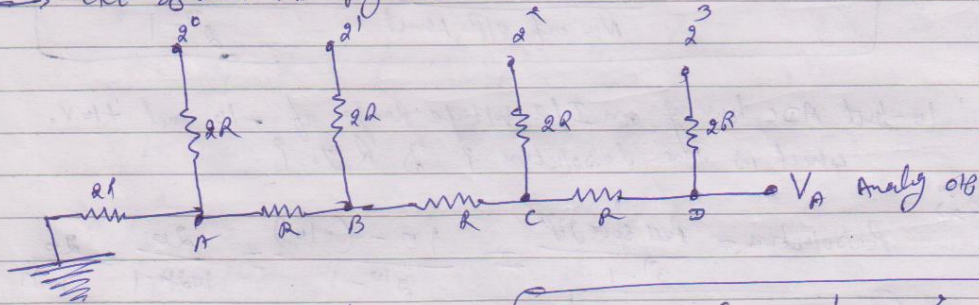


R-2R Ladder D/A Converter

→ It overcomes the drawback of Resistive network in which different value of resistances are used

→ but in case of R-2R ladder make the use of two values of resistor R and 2R.

→ ckt diagram in figure:



It uses the formula

$$V_A = \frac{V_0 2^0 + V_1 2^1 + V_2 2^2 + V_3 2^3}{2^n}$$

let us take an example:

if digital data is 0101 (4-bit data)


let us assume logic 0 = 0V

logic 1 = 16V

Digital input = 0101

$[2^4 = 16 \text{ for 4-bit}]$

Ckt diagram

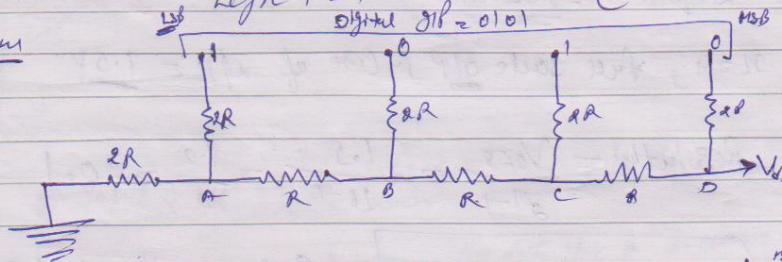


$$V_A = \frac{V_0 2^0 + V_1 2^1 + V_2 2^2 + V_3 2^3}{2^4}$$

$$V_A = \frac{1 \times 2^0 + 0 + 1 \times 2^2 + 0}{2^4} \Rightarrow \frac{16 \times 1 + 16 \times 1}{16}$$

MSB	LSB
0	1
1	0
0	1
1	0
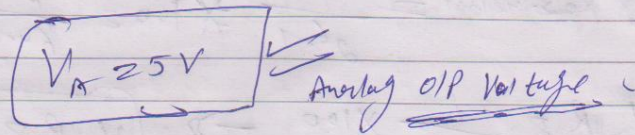
$$V_A = \frac{16+64}{16} = \frac{80}{16} = 5V$$



Q: A 6-bit R-2R Ladder D/A Converter has reference voltage of 6.5V. It means standard uncertainty

find out \Rightarrow (i) Resolution in Volt and Percentage

(ii) full scale voltage

(iii) O/P for 011100

Resolution: Resolution is the Reciprocal of number of discrete steps in the D/A O/Ps, Resolution

depends on the number of bits in digital systems. It is given by the eqn

$$R = \frac{1}{2^N - 1}, \text{ where } N = \text{number of bits}$$

% of Resolution is given by: $\left[\% R = \frac{1}{(2^N - 1)} \times 100 \right]$

but $N=1, 2, 3, \dots$ we get the appropriate percentage Resolution.

12)

Ans ① Resolution = $\frac{1}{2^n - 1}$ for $n=6$ for 6-bit

% Resolution = $\frac{1}{2^6 - 1} \times 100 = \frac{1}{63} \times 100$

% R = $\frac{1}{63} \times 100 \Rightarrow \boxed{\% R = 1.578\%}$

Resolution in volt = $\frac{V_{ref}}{2^n} = \frac{6.5}{2^6} = \frac{6.5}{64} = \boxed{0.1V}$

② full scale voltage (FSV) $\Rightarrow \boxed{FSV = V_{ref} \frac{(2^n - 1)}{2^n}}$

$= \frac{6.5 \times (2^6 - 1)}{2^6} = \frac{6.5 \times 63}{64}$

FSV = 6.398 $\approx \boxed{FSV = 6.4V}$

③ OP for 011100 is given by

$$V_{out} = \frac{V_0 2^0 + V_1 2^1 + V_2 2^2 + V_3 2^3 + V_4 2^4 + V_5 2^5}{2^6}$$

2 ⁵	2 ⁴	2 ³	2 ²	2 ¹	2 ⁰
0	1	1	1	0	0
V ₅	V ₄	V ₃	V ₂	V ₁	V ₀

and $n=6$

$$V_{out} = \frac{0 + 0 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0}{2^6}$$

$$V_{out} = \frac{6.5 \times 2^2 + 6.5 \times 2^3 + 6.5 \times 2^4}{64}$$

$$V_{out} = \frac{6.5 \times 28}{64} = 2.84V$$

$$\boxed{V_{out} = 2.84V}$$

here
Lysle 1 = +65V
Lysle = 0V
Below, V₂ = 65V