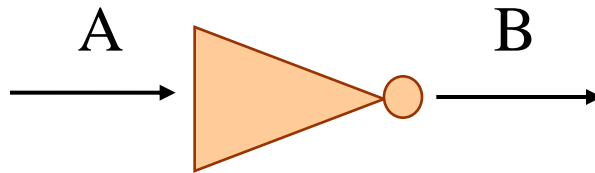


NOT Operator/Inverter Gate

- The NOT gate reverses the input



NOT Operator
Truth Table

A	B
0	1
1	0

- All digital computers are built using only three gate types: AND, OR, and NOT