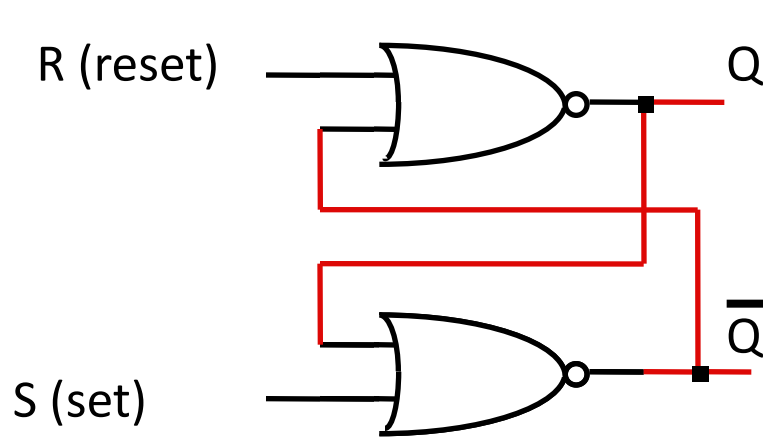


S-R Latch with NORs



S	R	Q	Q'	
1	1	0	0	Undefined
1	0	1	0	Set
0	1	0	1	Reset
0	0	0	1	Stable
		1	0	

S-R latch made from **cross-coupled** NORs


If $Q = 1$, set state

If $Q = 0$, reset state

Usually $S=0$ and $R=0$


$S=1$ and $R=1$ generates unpredictable results

S-R Latch with NANDs

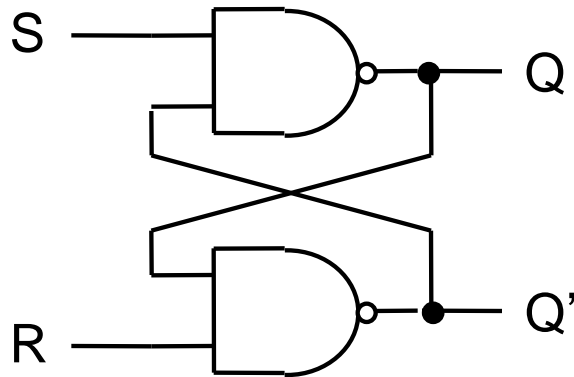



S	R	Q	Q'	
0	0	1	1	Disallowed
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	1	Store
		1	0	

Latch made from **cross-coupled** NANDs
Sometimes called S'-R' latch
Usually S=1 and R=1
S=0 and R=0 generates unpredictable results

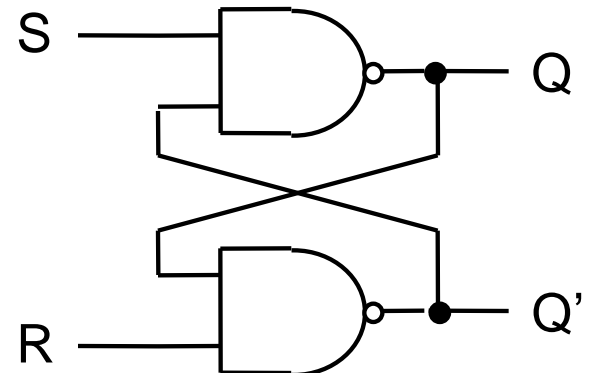



Case I: R

Inputs		Output	State
S	R	Q	
0	0	X	Invalid
0	1	0	Reset
1	0	1	Set
1	1	Q	No Change

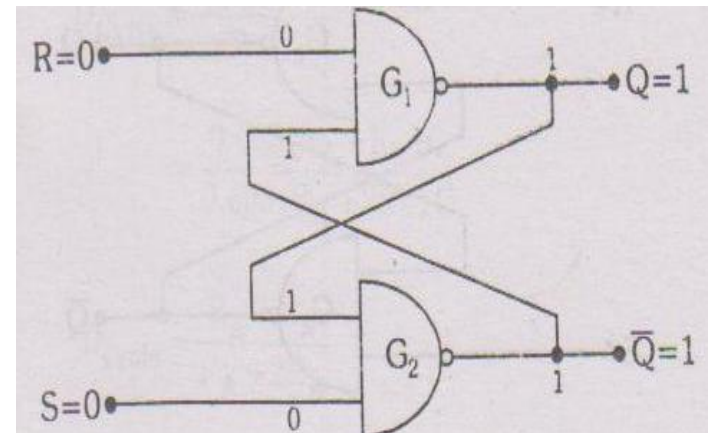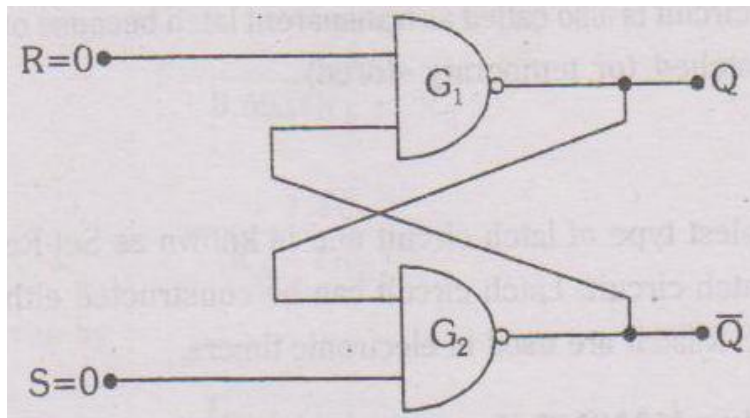



Case II: $S = 0$, $R = 1$

Inputs		Output	State
S	R	Q	
0	0	X	Invalid
0	1	0	Reset
1	0	1	Set
1	1	Q	No Change

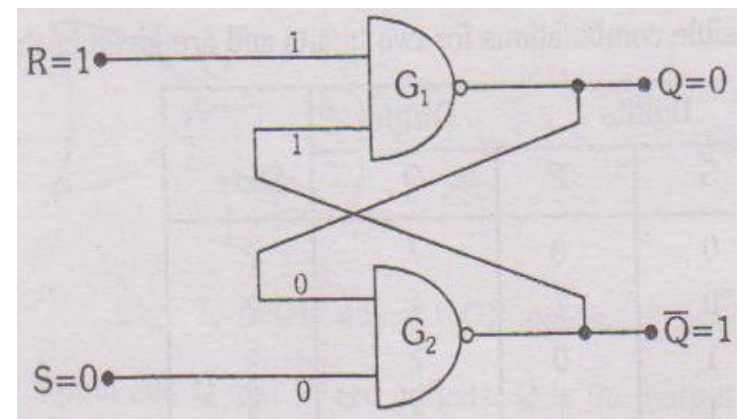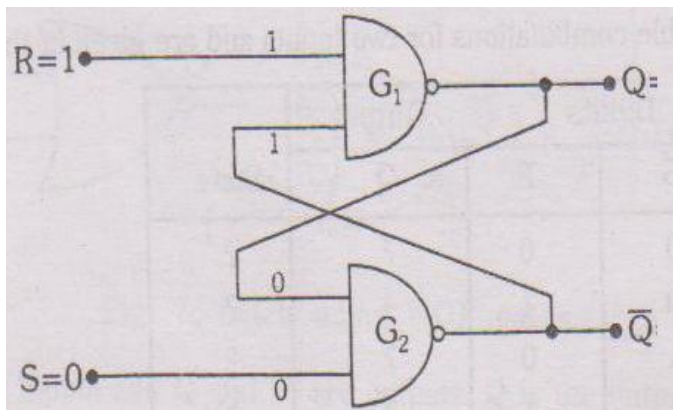



Case III: $S = 1$, $R = 0$

Inputs		Output	State
S	R	Q	
0	0	X	Invalid
0	1	0	Reset
1	0	1	Set
1	1	Q	No Change

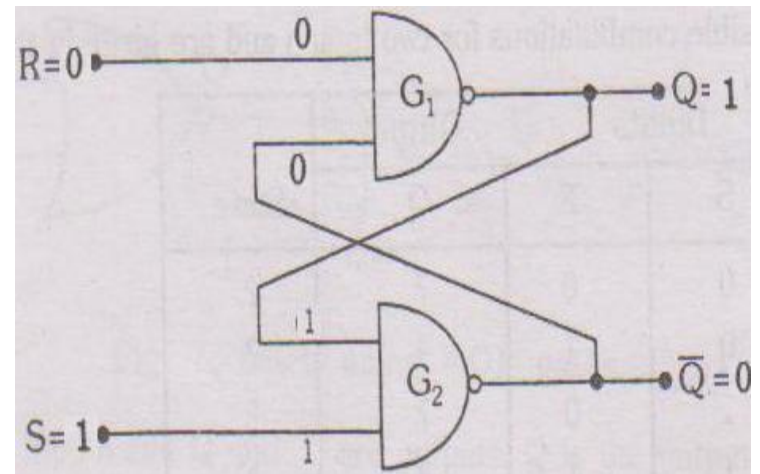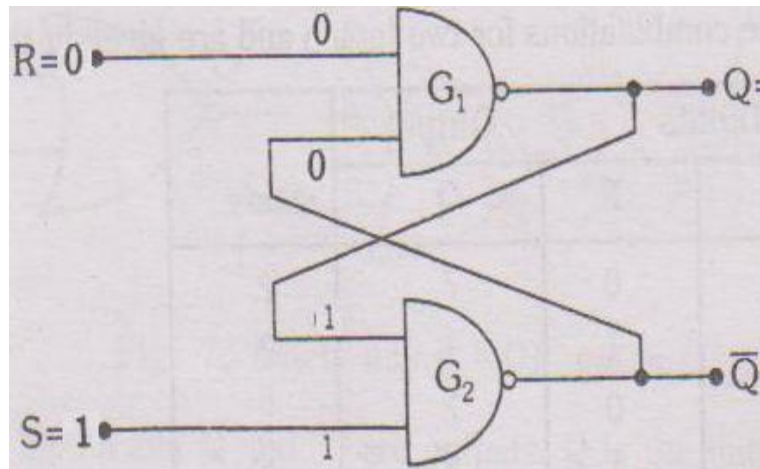


Case III: $S = 1$, $R = 0$


Inputs		Output	State
S	R	Q	
0	0	X	Invalid
0	1	0	Reset
1	0	1	Set
1	1	Q	No Change

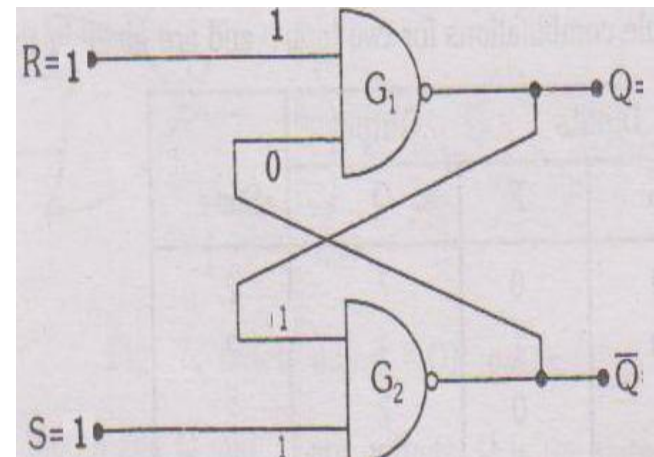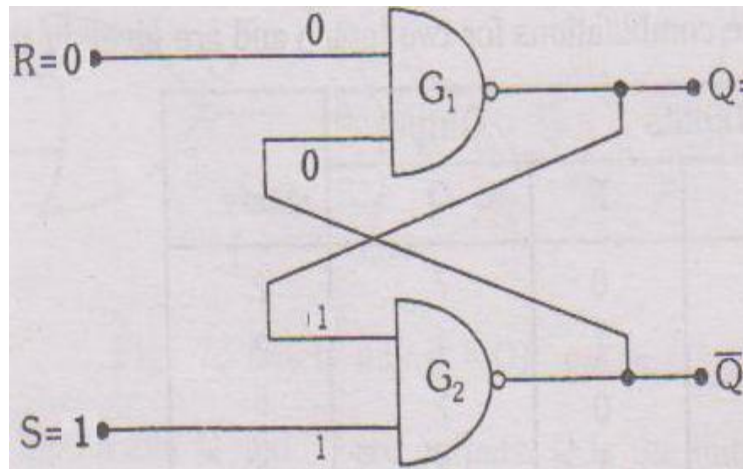

S-R Latches

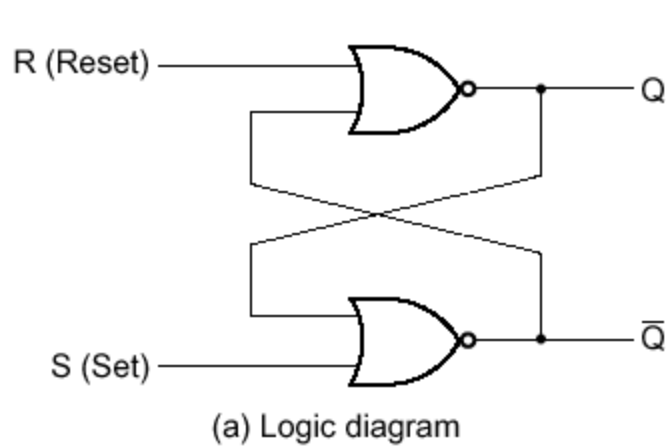

S	R	Q	Q'	
1	1	0	0	Undefined
1	0	1	0	Set
0	1	0	1	Reset
0	0	0	1	Stable
		1	0	

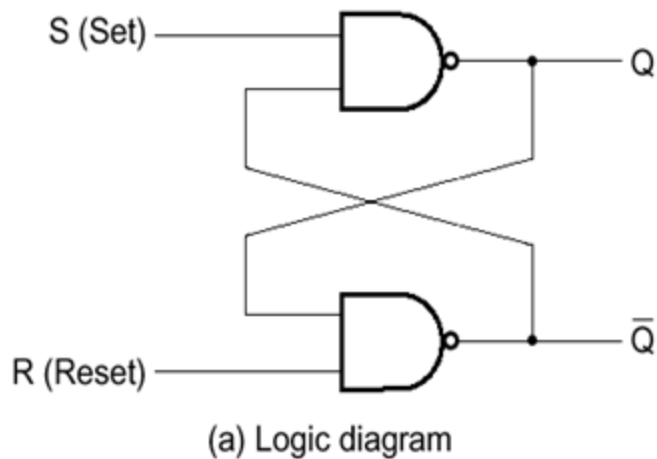

S	R	Q	Q'	
0	0	1	1	Disallowed
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	1	Store
		1	0	

Summary



- Latches are based on combinational gates (e.g. NAND, NOR)
- Latches store data even after data input has been removed
- S-R latches operate like cross-coupled inverters with control inputs (S = set, R = reset)
- With additional gates, an S-R latch can be converted to a D latch (D stands for data)
- D latch is simple to understand conceptually
 - When $C = 1$, data input D stored in latch and output as Q
 - When $C = 0$, data input D ignored and previous latch value output at Q
- Next time: more storage elements!

Gated latches(Clocked Flip Flop)

S-R Latch with control input

$C = 0$ disables all latch state changes

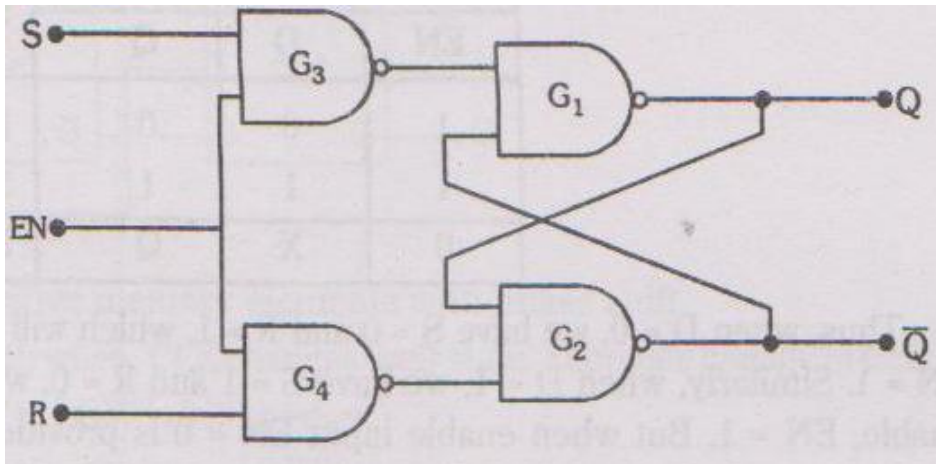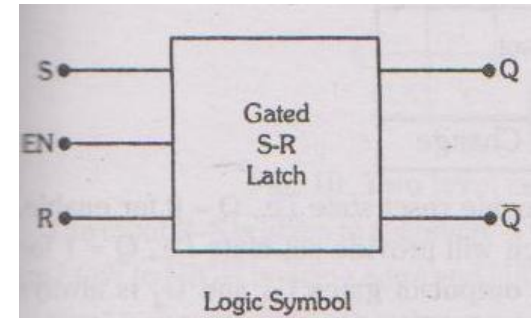Control signal **enables** data change when $C = 1$



C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table