 


# Master/Slave S-R Flip-Flop

- The *postponed output indicator* shows that the output signal does not change until the enable C input is negated.
- Flip-flops with this kind of behavior are called *pulse-triggered* flip-flops.
- $Q^* = S + R'Q$
- $SR = 0$


(a)



(b)

S	R	C	Q	QN
x	x	0	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		undef.	undef.


(c)

 

# Master/Slave J-K Flip-Flop

- The J and K inputs of the J-K flip-flop are analogous to the S and R inputs of the S-R flip-flop,
- except in the case where  $J=K=1$ . In this case the outputs of the J-K flip-flop will toggle to the opposite state.


(a)

 

(b)

J	K	C	Q	QN
x	x	0	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

(c)

 

# Master-Slave D Flip Flop

Consider two latches combined together

Only one  $C$  value active at a time

Output changes on **falling** edge of the clock

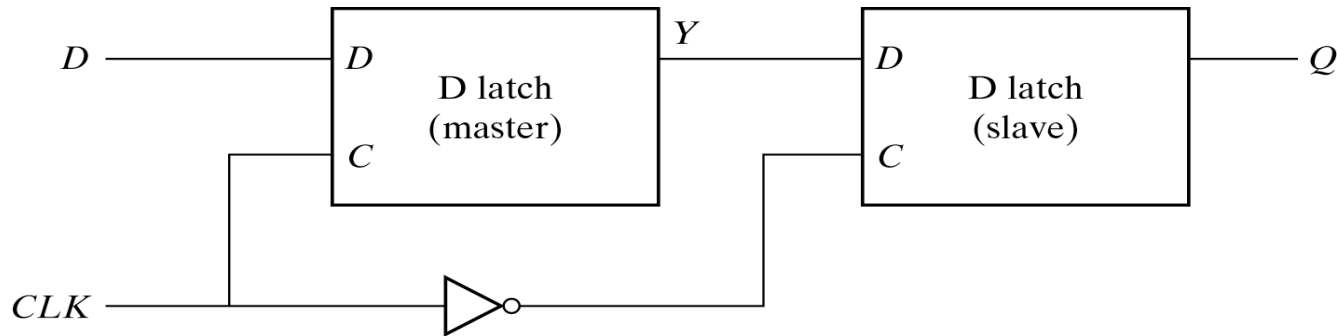


Fig. 5-9 Master-Slave  $D$  Flip-Flop